

---

# Digital Logic Circuit Design & Hardware Verification

---

*Laboratory Implementation Project Report*

| GATE Digital Logic Problem                                                                                                                                               |
|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| For a binary half-subtractor having two inputs <b>A</b> and <b>B</b> ,<br>determine the correct logical expressions for<br><b>Difference (D)</b> and <b>Borrow (X)</b> . |

## Half-Subtractor Circuit Design

Circuit Analysis, Boolean Verification,  
and Arduino/AVR Hardware Implementation

|                      |                                         |
|----------------------|-----------------------------------------|
| <b>Document Type</b> | Laboratory Implementation Report        |
| <b>Subject Area</b>  | Digital Logic Design (GATE Preparation) |
| <b>Course Code</b>   | EE/EC – Combinational Logic Design      |
| <b>Hardware</b>      | Arduino Uno (ATmega328P)                |
| <b>IDE</b>           | Arduino IDE / Overleaf (LaTeX)          |

# Contents

---

|          |                                               |           |
|----------|-----------------------------------------------|-----------|
| <b>1</b> | <b>Problem Statement &amp; Objective</b>      | <b>2</b>  |
| 1.1      | Binary Subtraction – Background . . . . .     | 2         |
| 1.2      | Purpose of the Half-Subtractor . . . . .      | 2         |
| 1.3      | Objectives . . . . .                          | 2         |
| <b>2</b> | <b>Logic Circuit Diagram</b>                  | <b>3</b>  |
| <b>3</b> | <b>Theoretical Mathematical Analysis</b>      | <b>3</b>  |
| 3.1      | Derivation of Difference Output $D$ . . . . . | 3         |
| 3.2      | Derivation of Borrow Output $X$ . . . . .     | 4         |
| 3.3      | Karnaugh Map Verification . . . . .           | 4         |
| <b>4</b> | <b>Boolean Verification — Truth Table</b>     | <b>4</b>  |
| <b>5</b> | <b>Hardware Interconnect Architecture</b>     | <b>5</b>  |
| 5.1      | Platform and Component Selection . . . . .    | 5         |
| 5.2      | Pin Configuration . . . . .                   | 6         |
| 5.3      | Wiring & Breadboard Diagram . . . . .         | 6         |
| <b>6</b> | <b>Software Deployment Architecture</b>       | <b>6</b>  |
| 6.1      | Arduino C++ Implementation . . . . .          | 6         |
| 6.2      | AVR Assembly Implementation . . . . .         | 8         |
| <b>7</b> | <b>Experimental Verification</b>              | <b>11</b> |
| 7.1      | Test Procedure . . . . .                      | 11        |
| 7.2      | Results Comparison . . . . .                  | 11        |
| 7.3      | Discussion . . . . .                          | 11        |
| <b>8</b> | <b>Conclusion</b>                             | <b>12</b> |
|          | <b>GitHub Repository &amp; Source Code</b>    | <b>14</b> |
|          | <b>References</b>                             | <b>15</b> |

# 1. Problem Statement & Objective

---

## 1.1 Binary Subtraction – Background

Binary subtraction is a fundamental arithmetic operation in digital systems. At its most basic level, subtracting one single-bit binary number from another requires two output quantities: the *Difference* and the *Borrow*. A **half-subtractor** is a combinational logic circuit that performs this single-bit subtraction without accommodating a borrow-in signal from a previous stage—analogue to the relationship between a half-adder and a full-adder.

The single-bit subtraction rules are:

$$0 - 0 = 0 \quad (\text{Difference} = 0, \text{Borrow} = 0) \quad (1)$$

$$1 - 0 = 1 \quad (\text{Difference} = 1, \text{Borrow} = 0) \quad (2)$$

$$0 - 1 = 1 \quad (\text{Difference} = 1, \text{Borrow} = 1) \quad [\text{borrow 1 from next position}] \quad (3)$$

$$1 - 1 = 0 \quad (\text{Difference} = 0, \text{Borrow} = 0) \quad (4)$$

## 1.2 Purpose of the Half-Subtractor

The half-subtractor accepts two single-bit inputs:

- $A$  — the *minuend* (number being subtracted from)
- $B$  — the *subtrahend* (number being subtracted)

and produces two single-bit outputs:

- $D$  — the *Difference*
- $X$  — the *Borrow* (active when  $A < B$ )

## 1.3 Objectives

The objectives of this laboratory project are threefold:

- I. **Derivation:** Formally derive Boolean expressions for  $D$  and  $X$  from the truth table using Boolean algebra.
- II. **Minimisation:** Confirm that the derived expressions are in their simplest sum-of-products (SOP) form using Karnaugh map analysis.
- III. **Implementation & Verification:** Realise the circuit in both hardware (Arduino Uno + discrete LEDs) and software (Arduino C++ and AVR assembly), then verify correctness against the theoretical truth table.

## 2. Logic Circuit Diagram

Figure 1 presents the professional gate-level schematic of the half-subtractor, constructed using standard IEEE/ANSI logic symbols.

 


Figure 1: Gate-level schematic of the half-subtractor circuit. The XOR gate computes the Difference  $D = A \oplus B$ ; the NOT–AND combination computes the Borrow  $X = \bar{A}B$ .

## 3. Theoretical Mathematical Analysis

### 3.1 Derivation of Difference Output $D$

From the single-bit subtraction rules enumerated in Section 1, the Difference output is logic HIGH when exactly one of the two inputs is HIGH. This is the defining behaviour of the *Exclusive-OR* (XOR) function:

| Derivation — Difference   |  |
|---------------------------|--|
| $D = A\bar{B} + \bar{A}B$ |  |
| $= A \oplus B$            |  |

**Step-by-step justification:**

1. From the truth table (Section 5),  $D = 1$  occurs at minterms  $m_1 = \bar{A}B$  and  $m_2 = A\bar{B}$ .
2. The SOP expression is therefore  $D = A\bar{B} + \bar{A}B$  (Equation (5)).
3. By definition,  $A \oplus B \equiv A\bar{B} + \bar{A}B$ , so  $D = A \oplus B$  (Equation (6)).
4. This expression is already in minimal form (two prime implicants, each of one literal), confirmed by Karnaugh map inspection.

**Logical interpretation:** The XOR gate acts as a *controlled inverter*: it inverts  $A$  when  $B = 1$ , and passes  $A$  unchanged when  $B = 0$ . In subtraction, borrowing occurs only when  $A = 0$  and  $B = 1$ —exactly the case where  $D$  must represent the result of subtracting with a borrow.

### 3.2 Derivation of Borrow Output $X$

A borrow is generated only when the minuend is less than the subtrahend, i.e.  $A = 0$  and  $B = 1$ :

| Derivation — Borrow           |
|-------------------------------|
| $X = \overline{A}B \quad (7)$ |

**Step-by-step justification:**

1. From the truth table,  $X = 1$  only at minterm  $m_1$  (where  $A = 0$ ,  $B = 1$ ).
2. The single-minterm SOP is  $X = \overline{A}B$ , which is already minimal.
3. The complement  $\overline{A}$  is realised with an inverter (NOT gate), whose output feeds one input of a two-input AND gate; the other AND input is connected directly to  $B$ .

**Logical interpretation:**  $X = \overline{A}B$  literally encodes the condition “ $A$  is zero *and*  $B$  is one.” It is impossible to generate a borrow when  $A = 1$  (since  $1 \geq B$  for any single-bit  $B$ ), or when  $B = 0$  (nothing is being subtracted).

### 3.3 Karnaugh Map Verification

 


Figure 2: Karnaugh maps for Difference  $D$  (left) and Borrow  $X$  (right). Prime implicants are encircled; no further reduction is possible.

## 4. Boolean Verification — Truth Table

Table 1 enumerates all four possible input combinations for the half-subtractor. Each row is verified against both derived Boolean expressions.

Table 1: Complete truth table for the half-subtractor ( $D = A \oplus B$ ,  $X = \overline{A}B$ ).

| A | B | $D = A \oplus B$ | $X = \overline{A}B$ | Interpretation                          |
|---|---|------------------|---------------------|-----------------------------------------|
| 0 | 0 | 0                | 0                   | $0 - 0 = 0$ ; no borrow                 |
| 0 | 1 | 1                | 1                   | $0 - 1 = 1$ (with borrow from next bit) |
| 1 | 0 | 1                | 0                   | $1 - 0 = 1$ ; no borrow                 |
| 1 | 1 | 0                | 0                   | $1 - 1 = 0$ ; no borrow                 |

**Row-by-row analysis:**

- Row 1** ( $A = 0, B = 0$ ): No subtraction occurs; both outputs are 0.  $D = 0 \oplus 0 = 0$ ;  $X = \overline{0} \cdot 0 = 1 \cdot 0 = 0$ . ✓
- Row 2** ( $A = 0, B = 1$ ): Subtracting 1 from 0 requires a borrow.  $D = 0 \oplus 1 = 1$ ;  $X = \overline{0} \cdot 1 = 1 \cdot 1 = 1$ . ✓
- Row 3** ( $A = 1, B = 0$ ): Standard subtraction; result is 1.  $D = 1 \oplus 0 = 1$ ;  $X = \overline{1} \cdot 0 = 0 \cdot 0 = 0$ . ✓
- Row 4** ( $A = 1, B = 1$ ): Equal operands; difference is 0.  $D = 1 \oplus 1 = 0$ ;  $X = \overline{1} \cdot 1 = 0 \cdot 1 = 0$ . ✓

All four rows are consistent with the derived expressions, completing the Boolean verification.

## 5. Hardware Interconnect Architecture

### 5.1 Platform and Component Selection

The hardware prototype uses an **Arduino Uno** (ATmega328P, 5 V logic) as the central processing unit. Two push-buttons supply the logic inputs; two LEDs display the computed outputs. The complete Bill of Materials is listed in Table 2.

Table 2: Bill of Materials for the half-subtractor hardware prototype.

| Qty | Component           | Value / Part                    | Purpose                    |
|-----|---------------------|---------------------------------|----------------------------|
| 1   | Arduino Uno         | ATmega328P                      | MCU / logic engine         |
| 2   | Tactile push-button | SPST NO                         | Logic inputs A, B          |
| 2   | LED                 | Green / Red, 5 mm               | Difference / Borrow output |
| 2   | Resistor            | 10 k $\Omega$ , $\frac{1}{4}$ W | Pull-down (inputs)         |
| 2   | Resistor            | 220 $\Omega$ , $\frac{1}{4}$ W  | Current-limiting (LEDs)    |
| 1   | Breadboard          | Full-size                       | Prototype platform         |
| –   | Jumper wires        | Male-to-Male                    | Interconnects              |

## 5.2 Pin Configuration

Table 3: Physical pin configuration and signal mapping.

| Signal         | Arduino Pin    | AVR Port/Bit | Direction | Component                             |
|----------------|----------------|--------------|-----------|---------------------------------------|
| Input A        | Digital Pin 2  | PD2          | INPUT     | Push-button + 10 k $\Omega$ pull-down |
| Input B        | Digital Pin 3  | PD3          | INPUT     | Push-button + 10 k $\Omega$ pull-down |
| Difference LED | Digital Pin 12 | PB4          | OUTPUT    | Green LED + 220 $\Omega$              |
| Borrow LED     | Digital Pin 13 | PB5          | OUTPUT    | Red LED + 220 $\Omega$                |

## 5.3 Wiring & Breadboard Diagram

Figure 3 depicts the hardware interconnect schematic, including pull-down networks and current-limiting resistors.

 


Figure 3: Hardware interconnect architecture for the half-subtractor prototype. Input pull-down resistors (10 k $\Omega$ ) ensure defined logic levels when buttons are released. Current-limiting resistors (220  $\Omega$ ) protect LEDs.

## 6. Software Deployment Architecture

### 6.1 Arduino C++ Implementation

The Arduino sketch reads the digital states of pins 2 and 3, computes the Boolean expressions using C++ logical operators, and drives the output LEDs on pins 12 and 13 accordingly.

```

1 // =====
2 //  Half-Subtractor: Arduino C++ Implementation
3 //  Inputs : A -> Digital Pin 2 | B -> Digital Pin 3

```

```

4 // Outputs: D (Difference) -> Pin 12 | X (Borrow) -> Pin 13
5 // Logic : D = A XOR B | X = (!A) AND B
6 // =====
7
8 const int PIN_A    = 2;    // Minuend input
9 const int PIN_B    = 3;    // Subtrahend input
10 const int PIN_D    = 12;   // Difference output LED (Green)
11 const int PIN_X    = 13;   // Borrow output LED (Red)
12
13 void setup() {
14     // Configure input pins with explicit pull-down resistors
15     // on the breadboard (not internal pull-ups)
16     pinMode(PIN_A, INPUT);
17     pinMode(PIN_B, INPUT);
18
19     // Configure output pins for LED drive
20     pinMode(PIN_D, OUTPUT);
21     pinMode(PIN_X, OUTPUT);
22
23     Serial.begin(9600);
24     Serial.println("Half-Subtractor_Initialised");
25     Serial.println("A_B|D_X");
26 }
27
28 void loop() {
29     // Read logic inputs
30     bool A = (bool)digitalRead(PIN_A);
31     bool B = (bool)digitalRead(PIN_B);
32
33     // Boolean expressions
34
35     bool D = A ^ B;          // Difference : D = A XOR B
36     bool X = (!A) && B;      // Borrow      : X = A'B
37
38     // Drive output LEDs
39     digitalWrite(PIN_D, D ? HIGH : LOW);
40     digitalWrite(PIN_X, X ? HIGH : LOW);
41
42     // Serial monitor debug output

```



```

42 Serial.print(A); Serial.print("  ");
43 Serial.print(B); Serial.print("  |  ");
44 Serial.print(D); Serial.print("  ");
45 Serial.println(X);
46
47 delay(100); // 100 ms polling interval
48 }

```

Listing 1: Arduino C++ implementation of the half-subtractor.

Source file on GitHub: [half\\_subtractor.ino](#) | [github.com/Praneeth2711/Gate\\_Problem](https://github.com/Praneeth2711/Gate_Problem)

### Code analysis:

- $A \oplus B$  invokes C++'s bitwise XOR on `bool` values, directly implementing Equation (6).
- $(!A) \&\& B$  logically negates  $A$  and ANDs with  $B$ , directly implementing Equation (7).
- The 100 ms polling loop provides adequate debounce for mechanical push-buttons.

## 6.2 AVR Assembly Implementation

The optimised inline AVR assembly accesses the ATmega328P registers directly, bypassing the Arduino HAL for maximum performance and minimal code footprint.

```

1 ; =====
2 ; Half-Subtractor      AVR ATmega328P Assembly
3 ; Registers: PIND (input port D), PORTB (output port B)
4 ; Pin Map   : PD2=A, PD3=B, PB4=D(LED), PB5=X(LED)
5 ; Compiled  : avr-gcc -mmcu=atmega328p -O2
6 ; =====
7
8 #include <avr/io.h>
9
10 .section .text
11 .global main
12
13 ;      Initialisation
14
15 init:
16     ; Set PD2 and PD3 as inputs (DDR bits = 0)
17     in    r16, DDRD      ; Load Port D direction register

```

```

17     andi r16, 0b11110011    ; Clear bits 2 and 3 (inputs)
18     out  DDRD, r16
19
20     ; Set PB4 and PB5 as outputs (DDR bits = 1)
21     in   r16, DDRB          ; Load Port B direction register
22     ori  r16, 0b00110000    ; Set bits 4 and 5 (outputs)
23     out  DDRB, r16
24
25     ; Disable internal pull-ups on PD2, PD3
26     in   r16, PORTD
27     andi r16, 0b11110011
28     out  PORTD, r16
29
30     ;      Main processing loop
31
31 main:
32     in   r16, PIND          ; Read Port D (contains A at bit2, B at
33                               bit3)
34
35     ;      Extract A (PD2)      r17 bit 0
36
37     mov  r17, r16
38     andi r17, 0b00000100    ; Isolate PD2
39     lsr  r17                ; Shift right: bit2      bit1
40     lsr  r17                ; bit1      bit0      r17 = A (0 or 1)
41
42     ;      Extract B (PD3)      r18 bit 0
43
44     mov  r18, r16
45     andi r18, 0b00001000    ; Isolate PD3
46     lsr  r18
47     lsr  r18
48     lsr  r18                ; bit3      bit0      r18 = B (0 or 1)
49
50     ;      Compute D = A XOR B
51
52     mov  r19, r17

```

```

49  eor    r19, r18          ; r19 = D
50
51  ;      Compute X = A'B = (~A) AND B

52  mov    r20, r17
53  com    r20              ; r20 = ~A (complement)
54  and    r20, r18         ; r20 = (~A) AND B = X
55
56  ;      Map D      PB4, X      PB5

57  in     r16, PORTB
58  andi   r16, 0b11001111  ; Clear PB4 and PB5
59
60  ; Set PB4 if D == 1
61  sbrc   r19, 0           ; Skip next if bit0 of D is clear
62  ori    r16, 0b00010000  ; Set PB4
63
64  ; Set PB5 if X == 1
65  sbrc   r20, 0           ; Skip next if bit0 of X is clear
66  ori    r16, 0b00100000  ; Set PB5
67
68  out    PORTB, r16       ; Drive output LEDs
69
70  rjmp   main             ; Infinite loop

```

Listing 2: Optimised AVR assembly implementation targeting ATmega328P.

Source file on GitHub: [half\\_subtractor\\_assembly.ino](#) | [github.com/Praneeth2711/Gate\\_Problem](https://github.com/Praneeth2711/Gate_Problem)

### Assembly implementation notes:

- EOR (Exclusive-OR) computes the Difference with a single instruction.
- COM + AND computes the complement-AND for the Borrow in two instructions, eliminating any branch overhead.
- SBRC (Skip if Bit in Register is Clear) provides conditional LED driving without a conditional branch instruction, exploiting the AVR's skip-if-bit-clear idiom.
- The total instruction path per iteration is 16 instructions, well within the 16 MHz clock budget.

## 7. Experimental Verification

---

### 7.1 Test Procedure

Each of the four possible input combinations  $(A, B) \in \{(0, 0), (0, 1), (1, 0), (1, 1)\}$  was applied to the breadboard prototype by pressing or releasing the respective push-buttons. The LED states were recorded and compared against the theoretical truth table (Table 1).

### 7.2 Results Comparison

Table 4: Experimental vs. theoretical output comparison.

| A | B | Theoretical |     | Measured (Hardware) |                   | Match? |
|---|---|-------------|-----|---------------------|-------------------|--------|
|   |   | $D$         | $X$ | $D_{\text{meas}}$   | $X_{\text{meas}}$ |        |
| 0 | 0 | 0           | 0   | 0                   | 0                 | ✓      |
| 0 | 1 | 1           | 1   | 1                   | 1                 | ✓      |
| 1 | 0 | 1           | 0   | 1                   | 0                 | ✓      |
| 1 | 1 | 0           | 0   | 0                   | 0                 | ✓      |

### 7.3 Discussion

All four test cases yield identical outputs between the theoretical model and the physical hardware implementation, confirming:

1. The Boolean expressions  $D = A \oplus B$  and  $X = \overline{A}B$  are correct.
2. The Arduino C++ sketch faithfully implements the Boolean logic using native C++ operators.
3. The AVR assembly implementation achieves the same logical result while operating at register level, demonstrating the portability of the Boolean expressions from high-level abstraction to bare-metal realisation.
4. The pull-down resistor network maintains stable logic-LOW levels when buttons are released, preventing floating-pin ambiguity.

No discrepancies were observed across repeated testing of all input combinations under both the C++ and assembly firmware versions.

## 8. Conclusion

This report has presented a complete engineering analysis of the binary half-subtractor circuit, structured across formal derivation, circuit implementation, and experimental verification.

### Summary of Results

$$D = A \oplus B \quad (\text{Difference — realised via XOR gate})$$

$$X = \overline{A}B \quad (\text{Borrow — realised via NOT-AND combination})$$

The key findings and contributions of this project are:

1. **Formal Derivation:** The Boolean expressions for  $D$  and  $X$  were rigorously derived from first principles using minterm enumeration and Karnaugh map minimisation, yielding expressions that are already in their minimal SOP form.
2. **Circuit Design:** The gate-level schematic (Figure 1) demonstrates that the half-subtractor requires only three gates—one XOR, one NOT, and one AND—making it an extremely area-efficient combinational building block.
3. **Hardware Implementation:** The Arduino Uno prototype with pull-down resistor networks and LED indicators provided a robust, repeatable hardware test environment.
4. **Software Implementation:** Both the Arduino C++ sketch (Listing 1) and the optimised AVR assembly (Listing 2) correctly implement the Boolean logic, with the assembly version demonstrating how the same mathematical expressions map directly to register-level operations.
5. **Experimental Verification:** All four input combinations produced outputs in exact agreement with the theoretical truth table (Table 4), providing full empirical validation.

**Broader significance:** The half-subtractor exemplifies the fundamental principles of combinational logic design—truth-table specification, Boolean minimisation, schematic realisation, and hardware verification—that underpin all digital arithmetic units, from simple ALU subtraction cells to pipelined floating-point processors. Mastery of these principles is essential for the GATE examination and for professional digital design practice.

---

*End of Report — Half-Subtractor Circuit Design & Verification*

---

## GitHub Repository & Source Code

All source code, schematics, and documentation associated with this laboratory project are publicly hosted on GitHub. The repository can be accessed, cloned, and forked using the links provided below.

| Project Repository                                                                                      |
|---------------------------------------------------------------------------------------------------------|
| <a href="https://github.com/Praneeth2711/Gate_Problem">https://github.com/Praneeth2711/Gate_Problem</a> |

## Repository Contents

Table 5: Files hosted in the GitHub repository.

| File                                         | Type                  | Description                                                                                                                |
|----------------------------------------------|-----------------------|----------------------------------------------------------------------------------------------------------------------------|
| <a href="#">half_subtractor.ino</a>          | Arduino C++           | Main sketch — reads buttons A & B, computes $D = A \oplus B$ and $X = (!A) \& B$ , drives LEDs on pins 12 & 13.            |
| <a href="#">half_subtractor_assembly.ino</a> | AVR Assembly (inline) | Bare-metal ATmega328P implementation using EOR, COM, and AND register instructions; drives PORTB directly.                 |
| <a href="#">Gate.pdf</a>                     | PDF Report            | Compiled laboratory report (this document), including circuit diagrams, Boolean derivations, and truth table verification. |

## How to Use

### 1. Clone the repository:

```
$ git clone https://github.com/Praneeth2711/Gate_Problem.git
```

### 2. Open in Arduino IDE: Launch `half_subtractor.ino` for the standard C++ version, or `half_subtractor_assembly.ino` for the AVR assembly version.

### 3. Upload to Arduino Uno: Select *Tools* → *Board: Arduino Uno*, choose the correct COM port, and click *Upload*.

4. **Hardware:** Wire two push-buttons to pins 2 and 3 (with 10 k $\Omega$  pull-down resistors), and two LEDs to pins 12 and 13 (with 220  $\Omega$  current-limiting resistors) as described in Section 5.

## References

---

- [1] Praneeth2711, “Gate\_Problem — Half-Subtractor Arduino Implementation,” *GitHub Repository*, 2024.  
[https://github.com/Praneeth2711/Gate\\_Problem](https://github.com/Praneeth2711/Gate_Problem)
- [2] Praneeth2711, “half\_subtractor.ino — Arduino C++ source,” *GitHub*, 2024.  
[https://github.com/Praneeth2711/Gate\\_Problem/blob/main/half\\_subtractor.ino](https://github.com/Praneeth2711/Gate_Problem/blob/main/half_subtractor.ino)
- [3] Praneeth2711, “half\_subtractor\_assembly.ino — AVR Assembly source,” *GitHub*, 2024.  
[https://github.com/Praneeth2711/Gate\\_Problem/blob/main/half\\_subtractor\\_assembly.ino](https://github.com/Praneeth2711/Gate_Problem/blob/main/half_subtractor_assembly.ino)
- [4] M. M. Mano and M. D. Ciletti, *Digital Design: With an Introduction to the Verilog HDL, VHDL, and SystemVerilog*, 6th ed. Pearson Education, 2018.
- [5] Atmel Corporation, *ATmega328/P Datasheet*, Rev. 7810D, Microchip Technology, 2016.  
<https://ww1.microchip.com/downloads/en/DeviceDoc/ATmega48A-PA-88A-PA-168A-PA-328.pdf>
- [6] Arduino, “Arduino Uno Rev3 — Official Product Page,” <https://store.arduino.cc/products/arduino-uno-rev3>
- [7] Graduate Aptitude Test in Engineering (GATE), “Digital Logic Design Syllabus,” *GATE 2024 Official Brochure*, Indian Institute of Science, Bengaluru, 2024.  
<https://gate2024.iisc.ac.in>