
Digital Logic Circuit Design & Hardware Verification

Laboratory Implementation Project Report

GATE Digital Logic Problem
For a binary half-subtractor having two inputs A and B , determine the correct logical expressions for Difference (D) and Borrow (X) .

Half-Subtractor Circuit Design

Circuit Analysis, Boolean Verification,
and Arduino/AVR Hardware Implementation

Document Type	Laboratory Implementation Report
Subject Area	Digital Logic Design (GATE Preparation)
Course Code	EE/EC – Combinational Logic Design
Hardware	Arduino Uno (ATmega328P)
IDE	Arduino IDE / Overleaf (LaTeX)

Contents

1 Problem Statement & Objective	2
1.1 Binary Subtraction – Background	2
1.2 Purpose of the Half-Subtractor	2
1.3 Objectives	2
2 Logic Circuit Diagram	3
3 Theoretical Mathematical Analysis	3
3.1 Derivation of Difference Output D	3
3.2 Derivation of Borrow Output X	4
3.3 Karnaugh Map Verification	4
4 Boolean Verification — Truth Table	4
5 Hardware Interconnect Architecture	5
5.1 Platform and Component Selection	5
5.2 Pin Configuration	6
5.3 Wiring & Breadboard Diagram	6
6 Software Deployment Architecture	6
6.1 Arduino C++ Implementation	6
6.2 AVR Assembly Implementation	7
7 Experimental Verification	7
7.1 Test Procedure	7
7.2 Results Comparison	7
7.3 Discussion	7
8 Conclusion	8
GitHub Repository & Source Code	10
References	11

1. Problem Statement & Objective

1.1 Binary Subtraction – Background

Binary subtraction is a fundamental arithmetic operation in digital systems. At its most basic level, subtracting one single-bit binary number from another requires two output quantities: the *Difference* and the *Borrow*. A **half-subtractor** is a combinational logic circuit that performs this single-bit subtraction without accommodating a borrow-in signal from a previous stage—analogue to the relationship between a half-adder and a full-adder.

The single-bit subtraction rules are:

$$0 - 0 = 0 \quad (\text{Difference} = 0, \text{Borrow} = 0) \quad (1)$$

$$1 - 0 = 1 \quad (\text{Difference} = 1, \text{Borrow} = 0) \quad (2)$$

$$0 - 1 = 1 \quad (\text{Difference} = 1, \text{Borrow} = 1) \quad [\text{borrow 1 from next position}] \quad (3)$$

$$1 - 1 = 0 \quad (\text{Difference} = 0, \text{Borrow} = 0) \quad (4)$$

1.2 Purpose of the Half-Subtractor

The half-subtractor accepts two single-bit inputs:

- A — the *minuend* (number being subtracted from)
- B — the *subtrahend* (number being subtracted)

and produces two single-bit outputs:

- D — the *Difference*
- X — the *Borrow* (active when $A < B$)

1.3 Objectives

The objectives of this laboratory project are threefold:

- I. **Derivation:** Formally derive Boolean expressions for D and X from the truth table using Boolean algebra.
- II. **Minimisation:** Confirm that the derived expressions are in their simplest sum-of-products (SOP) form using Karnaugh map analysis.
- III. **Implementation & Verification:** Realise the circuit in both hardware (Arduino Uno + discrete LEDs) and software (Arduino C++ and AVR assembly), then verify correctness against the theoretical truth table.

2. Logic Circuit Diagram

Figure 1 presents the professional gate-level schematic of the half-subtractor, constructed using standard IEEE/ANSI logic symbols.

 


Figure 1: Gate-level schematic of the half-subtractor circuit. The XOR gate computes the Difference $D = A \oplus B$; the NOT–AND combination computes the Borrow $X = \bar{A}B$.

3. Theoretical Mathematical Analysis

3.1 Derivation of Difference Output D

From the single-bit subtraction rules enumerated in Section 1, the Difference output is logic HIGH when exactly one of the two inputs is HIGH. This is the defining behaviour of the *Exclusive-OR* (XOR) function:

Derivation — Difference	
$D = A\bar{B} + \bar{A}B$	
$= A \oplus B$	

Step-by-step justification:

1. From the truth table (Section 5), $D = 1$ occurs at minterms $m_1 = \bar{A}B$ and $m_2 = A\bar{B}$.
2. The SOP expression is therefore $D = A\bar{B} + \bar{A}B$ (Equation (5)).
3. By definition, $A \oplus B \equiv A\bar{B} + \bar{A}B$, so $D = A \oplus B$ (Equation (6)).
4. This expression is already in minimal form (two prime implicants, each of one literal), confirmed by Karnaugh map inspection.

Logical interpretation: The XOR gate acts as a *controlled inverter*: it inverts A when $B = 1$, and passes A unchanged when $B = 0$. In subtraction, borrowing occurs only when $A = 0$ and $B = 1$ —exactly the case where D must represent the result of subtracting with a borrow.

3.2 Derivation of Borrow Output X

A borrow is generated only when the minuend is less than the subtrahend, i.e. $A = 0$ and $B = 1$:

Derivation — Borrow
$X = \overline{A}B \quad (7)$

Step-by-step justification:

1. From the truth table, $X = 1$ only at minterm m_1 (where $A = 0$, $B = 1$).
2. The single-minterm SOP is $X = \overline{A}B$, which is already minimal.
3. The complement $\overline{A}$ is realised with an inverter (NOT gate), whose output feeds one input of a two-input AND gate; the other AND input is connected directly to B .

Logical interpretation: $X = \overline{A}B$ literally encodes the condition “ A is zero *and* B is one.” It is impossible to generate a borrow when $A = 1$ (since $1 \geq B$ for any single-bit B), or when $B = 0$ (nothing is being subtracted).

3.3 Karnaugh Map Verification

 


Figure 2: Karnaugh maps for Difference D (left) and Borrow X (right). Prime implicants are encircled; no further reduction is possible.

4. Boolean Verification — Truth Table

Table 1 enumerates all four possible input combinations for the half-subtractor. Each row is verified against both derived Boolean expressions.

Table 1: Complete truth table for the half-subtractor ($D = A \oplus B$, $X = \overline{A}B$).

A	B	$D = A \oplus B$	$X = \overline{A}B$	Interpretation
0	0	0	0	$0 - 0 = 0$; no borrow
0	1	1	1	$0 - 1 = 1$ (with borrow from next bit)
1	0	1	0	$1 - 0 = 1$; no borrow
1	1	0	0	$1 - 1 = 0$; no borrow

Row-by-row analysis:

- Row 1** ($A = 0, B = 0$): No subtraction occurs; both outputs are 0. $D = 0 \oplus 0 = 0$; $X = \overline{0} \cdot 0 = 1 \cdot 0 = 0$. ✓
- Row 2** ($A = 0, B = 1$): Subtracting 1 from 0 requires a borrow. $D = 0 \oplus 1 = 1$; $X = \overline{0} \cdot 1 = 1 \cdot 1 = 1$. ✓
- Row 3** ($A = 1, B = 0$): Standard subtraction; result is 1. $D = 1 \oplus 0 = 1$; $X = \overline{1} \cdot 0 = 0 \cdot 0 = 0$. ✓
- Row 4** ($A = 1, B = 1$): Equal operands; difference is 0. $D = 1 \oplus 1 = 0$; $X = \overline{1} \cdot 1 = 0 \cdot 1 = 0$. ✓

All four rows are consistent with the derived expressions, completing the Boolean verification.

5. Hardware Interconnect Architecture

5.1 Platform and Component Selection

The hardware prototype uses an **Arduino Uno** (ATmega328P, 5 V logic) as the central processing unit. Two push-buttons supply the logic inputs; two LEDs display the computed outputs. The complete Bill of Materials is listed in Table 2.

Table 2: Bill of Materials for the half-subtractor hardware prototype.

Qty	Component	Value / Part	Purpose
1	Arduino Uno	ATmega328P	MCU / logic engine
2	Tactile push-button	SPST NO	Logic inputs A, B
2	LED	Green / Red, 5 mm	Difference / Borrow output
2	Resistor	10 k Ω , $\frac{1}{4}$ W	Pull-down (inputs)
2	Resistor	220 Ω , $\frac{1}{4}$ W	Current-limiting (LEDs)
1	Breadboard	Full-size	Prototype platform
–	Jumper wires	Male-to-Male	Interconnects

5.2 Pin Configuration

Table 3: Physical pin configuration and signal mapping.

Signal	Arduino Pin	AVR Port/Bit	Direction	Component
Input A	Digital Pin 2	PD2	INPUT	Push-button + 10 k Ω pull-down
Input B	Digital Pin 3	PD3	INPUT	Push-button + 10 k Ω pull-down
Difference LED	Digital Pin 12	PB4	OUTPUT	Green LED + 220 Ω
Borrow LED	Digital Pin 13	PB5	OUTPUT	Red LED + 220 Ω

5.3 Wiring & Breadboard Diagram

Figure 3 depicts the hardware interconnect schematic, including pull-down networks and current-limiting resistors.

 


Figure 3: Hardware interconnect architecture for the half-subtractor prototype. Input pull-down resistors (10 k Ω) ensure defined logic levels when buttons are released. Current-limiting resistors (220 Ω) protect LEDs.

6. Software Deployment Architecture

Two firmware implementations are provided for this project — an Arduino C++ sketch and an optimised AVR assembly version. Both are hosted on GitHub and can be downloaded or cloned directly. Click the link for each file below to open it in the repository.

6.1 Arduino C++ Implementation

The Arduino sketch reads inputs A and B from digital pins 2 and 3, computes $D = A \oplus B$ and $X = \overline{A}B$ using native C++ operators, and drives the Difference and Borrow LEDs on

pins 12 and 13.

Arduino C++ Source Code

[half_subtractor.ino](#)

Click the link above to open the source file on GitHub

6.2 AVR Assembly Implementation

The AVR assembly version accesses the ATmega328P hardware registers directly — reading inputs from PIND and writing outputs to PORTB — for maximum performance with minimal code footprint.

AVR Assembly Source Code

[half_subtractor_assembly.ino](#)

Click the link above to open the source file on GitHub

7. Experimental Verification

7.1 Test Procedure

Each of the four possible input combinations $(A, B) \in \{(0, 0), (0, 1), (1, 0), (1, 1)\}$ was applied to the breadboard prototype by pressing or releasing the respective push-buttons. The LED states were recorded and compared against the theoretical truth table (Table 1).

7.2 Results Comparison

Table 4: Experimental vs. theoretical output comparison.

A	B	Theoretical		Measured (Hardware)		Match?
		D	X	D_{meas}	X_{meas}	
0	0	0	0	0	0	✓
0	1	1	1	1	1	✓
1	0	1	0	1	0	✓
1	1	0	0	0	0	✓

7.3 Discussion

All four test cases yield identical outputs between the theoretical model and the physical hardware implementation, confirming:

1. The Boolean expressions $D = A \oplus B$ and $X = \overline{A}B$ are correct.
2. The Arduino C++ sketch faithfully implements the Boolean logic using native C++ operators.
3. The AVR assembly implementation achieves the same logical result while operating at register level, demonstrating the portability of the Boolean expressions from high-level abstraction to bare-metal realisation.
4. The pull-down resistor network maintains stable logic-LOW levels when buttons are released, preventing floating-pin ambiguity.

No discrepancies were observed across repeated testing of all input combinations under both the C++ and assembly firmware versions.

8. Conclusion

This report has presented a complete engineering analysis of the binary half-subtractor circuit, structured across formal derivation, circuit implementation, and experimental verification.

Summary of Results

$D = A \oplus B$	(Difference — realised via XOR gate)
$X = \overline{A}B$	(Borrow — realised via NOT-AND combination)

The key findings and contributions of this project are:

1. **Formal Derivation:** The Boolean expressions for D and X were rigorously derived from first principles using minterm enumeration and Karnaugh map minimisation, yielding expressions that are already in their minimal SOP form.
2. **Circuit Design:** The gate-level schematic (Figure 1) demonstrates that the half-subtractor requires only three gates—one XOR, one NOT, and one AND—making it an extremely area-efficient combinational building block.
3. **Hardware Implementation:** The Arduino Uno prototype with pull-down resistor networks and LED indicators provided a robust, repeatable hardware test environment.

4. **Software Implementation:** Both the Arduino C++ sketch and the optimised AVR assembly (available on GitHub) correctly implement the Boolean logic, with the assembly version demonstrating how the same mathematical expressions map directly to register-level operations.
5. **Experimental Verification:** All four input combinations produced outputs in exact agreement with the theoretical truth table (Table 4), providing full empirical validation.

Broader significance: The half-subtractor exemplifies the fundamental principles of combinational logic design—truth-table specification, Boolean minimisation, schematic realisation, and hardware verification—that underpin all digital arithmetic units, from simple ALU subtraction cells to pipelined floating-point processors. Mastery of these principles is essential for the GATE examination and for professional digital design practice.

End of Report — Half-Subtractor Circuit Design & Verification

GitHub Repository & Source Code

All source code, schematics, and documentation associated with this laboratory project are publicly hosted on GitHub. The repository can be accessed, cloned, and forked using the links provided below.

Project Repository
https://github.com/Praneeth2711/Gate_Problem

Repository Contents

Table 5: Files hosted in the GitHub repository.

File	Type	Description
half_subtractor.ino	Arduino C++	Main sketch — reads buttons A & B, computes $D = A \oplus B$ and $X = (!A) \& B$, drives LEDs on pins 12 & 13.
half_subtractor_assembly.ino	AVR Assembly (inline)	Bare-metal ATmega328P implementation using EOR, COM, and AND register instructions; drives PORTB directly.
Gate.pdf	PDF Report	Compiled laboratory report (this document), including circuit diagrams, Boolean derivations, and truth table verification.

How to Use

1. Clone the repository:

```
$ git clone https://github.com/Praneeth2711/Gate_Problem.git
```

2. Open in Arduino IDE: Launch `half_subtractor.ino` for the standard C++ version, or `half_subtractor_assembly.ino` for the AVR assembly version.

3. Upload to Arduino Uno: Select *Tools* → *Board: Arduino Uno*, choose the correct COM port, and click *Upload*.

4. **Hardware:** Wire two push-buttons to pins 2 and 3 (with 10 k Ω pull-down resistors), and two LEDs to pins 12 and 13 (with 220 Ω current-limiting resistors) as described in Section 5.

References

- [1] Praneeth2711, “Gate_Problem — Half-Subtractor Arduino Implementation,” *GitHub Repository*.
https://github.com/Praneeth2711/Gate_Problem
- [2] Praneeth2711, “Arduino C++ source — half_subtractor.ino,” *GitHub*.
https://github.com/Praneeth2711/Gate_Problem/blob/main/half_subtractor.ino
- [3] Praneeth2711, “AVR Assembly source — half_subtractor_assembly.ino,” *GitHub*.
https://github.com/Praneeth2711/Gate_Problem/blob/main/half_subtractor_assembly.ino